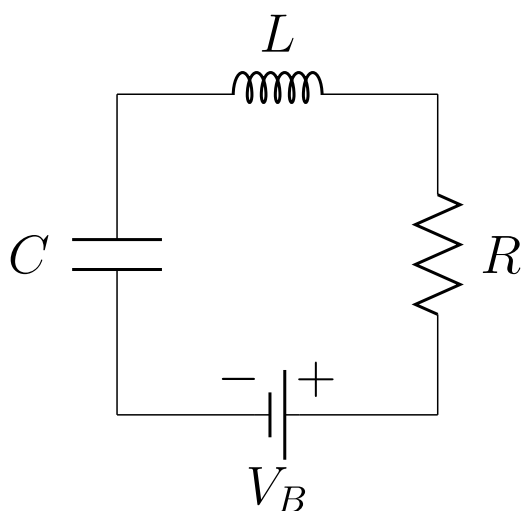


[Course](#) > [3. Extending the model](#) > [3.2 Practice problem \(Clock!\)](#) > Mathematical model

Mathematical model

🔖 Bookmark this page

For a base clock for a computer, we want to build an *LC-oscillator* that generates **100 MHz** oscillations.



The components that are given are:

- a 5V battery: $V_B = 5\text{ V}$,
- an inductor: $L = 0.004\text{ }\mu\text{H}$,
- the resistance: $R = 0.1\text{ }\Omega$.

Our problem is

*Find the capacitance C of the capacitor ($[C] = \text{henry}$) such that the current in the electrical circuit oscillates with a frequency of **100 MHz**.*

The following physical laws relate the current $I(t)$ running in the circuit (measured in ampere), the charge on (one side of) the capacitor $Q(t)$ (in coulomb) and the voltage drops over the different elements (in volts).

The current, $I(t)$, is related to the charge on the capacitor, $Q(t)$, according to

$$I(t) = \frac{dQ}{dt}.$$

The voltage drop over the capacitor, $V(t)$, is related to the charge on the capacitor by:

$$V(t) = \frac{Q(t)}{C}.$$

The voltage drop over the inductor, $V_L(t)$, is related to the change in the current:

$$V_L(t) = L \frac{dI}{dt}.$$

And an expression for voltage drop over the resistor, $V_R(t)$ is given by: $V_R(t) = RI(t)$.

Kirchhoff's voltage law states that the voltage drop around a loop in a circuit equals zero:

$$V + V_L + V_R - V_B = 0.$$

There are different options for a set of dependent variables to calculate in. We choose to calculate in current $I(t)$ and the voltage drop over the capacitor $V(t)$.

Exercise A

1/1 point (graded)

Eliminate the charge from the first two physical laws and derive a relation between V and I :

☐ $\frac{dV}{dt} = I(t)$

☐ $C \frac{dI}{dt} = V(t)$

☒ $C \frac{dV}{dt} = I(t)$ ✓

Submit

You have used 1 of 1 attempt

i Answers are displayed within the problem

Exercise B

1/1 point (graded)

Use the last three physical laws to derive the second relation between V and I :

☒ $L \frac{dI}{dt} = V_B - R I(t) - V(t)$ ✓

☐ $\frac{L}{C} \frac{dI}{dt} = C V_B - R I(t) - V(t)$

☐ $L \frac{dI}{dt} = \frac{V_B}{C} + R I(t) + V(t)$

You have used 1 of 1 attempt

i Answers are displayed within the problem

Exercise C

1/1 point (graded)

 Keyboard Help

PROBLEM

Combine the two differential equations from exercises A and B into one system of equations of the form shown below.

$$\frac{d\vec{X}}{dt} = \begin{bmatrix} 0 & 1/C \\ -1/L & -R/L \end{bmatrix} \vec{X} + \begin{bmatrix} 0 \\ V_B/L \end{bmatrix},$$

with $\vec{X} = \begin{bmatrix} I \\ V \end{bmatrix}$,

$$A = \begin{bmatrix} 0 & 1/C \\ -1/L & -R/L \end{bmatrix},$$

and $\vec{b} = \begin{bmatrix} 0 \\ V_B/L \end{bmatrix}.$

Submit

You have used 1 of 3 attempts.



Reset



Show Answer

FEEDBACK

✓ Correctly placed 6 items.

✓ Good work! You have correctly formulated the vector differential equation.


✓ Your highest score is 1.0

Initial conditions

We will assume that before $t = 0$, there is no current, and the capacitor is not charged. Only at $t = 0$, the battery is connected. The initial conditions are then

$$V(0) = 0, \quad I(0) = 0.$$

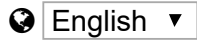Eager to start simulating? On the next page, first a scaling, and then you can start up Euler's method!



© 2012-2017 edX Inc. All rights reserved except where noted. EdX, Open edX and the edX and Open EdX logos are registered trademarks or trademarks of edX Inc. | 粤ICP备17044299号-2

